


ATED POWER SUPPLY (230V AC TO 5V DC)

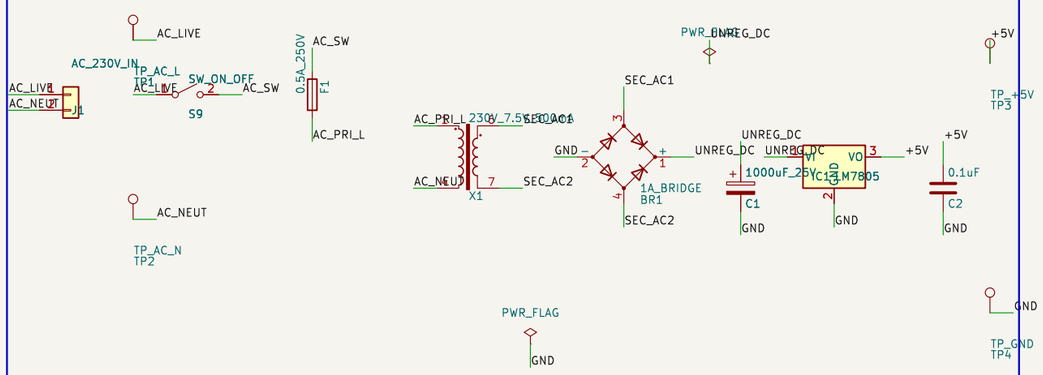


LOCKOUT & BUZZER DRIVER

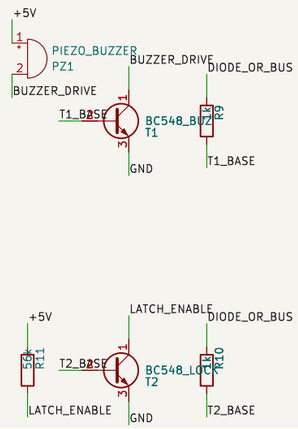

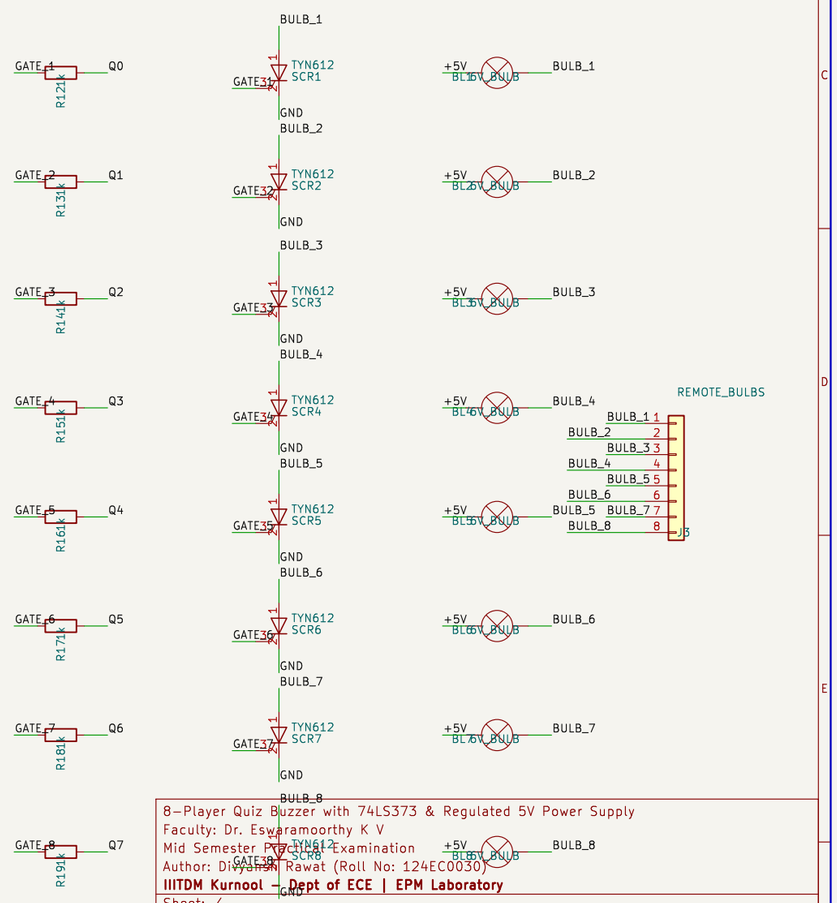
SECTION 4: ANNUNCIATOR STAGE (SCR1–SCR8 & BL1–BL8)



AYER INPUTS (S1–S8 & PULL-DOWNS)

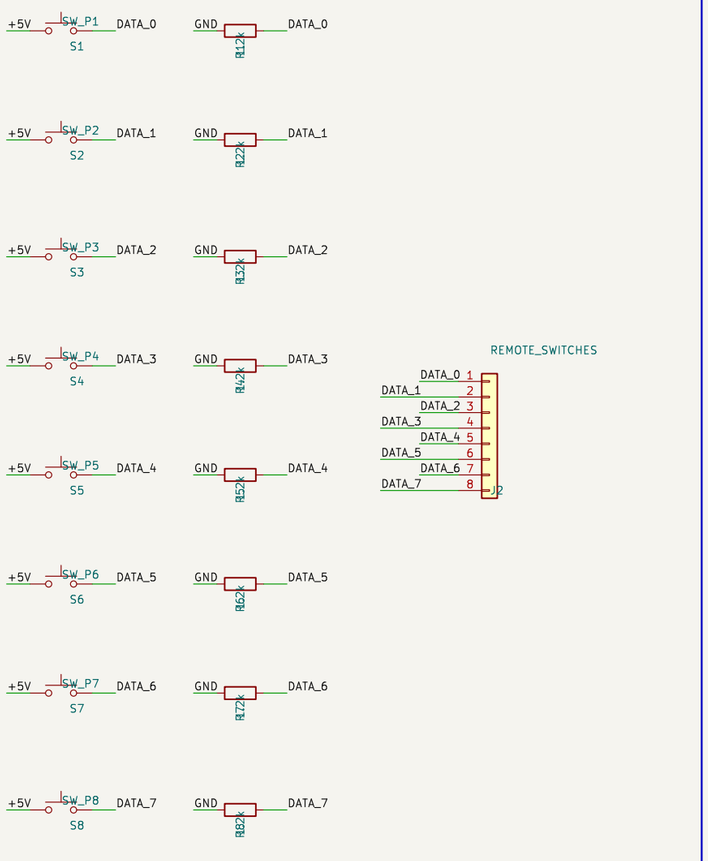

SECTION 3: 74LS373 LATCH & DIODE OR-ING

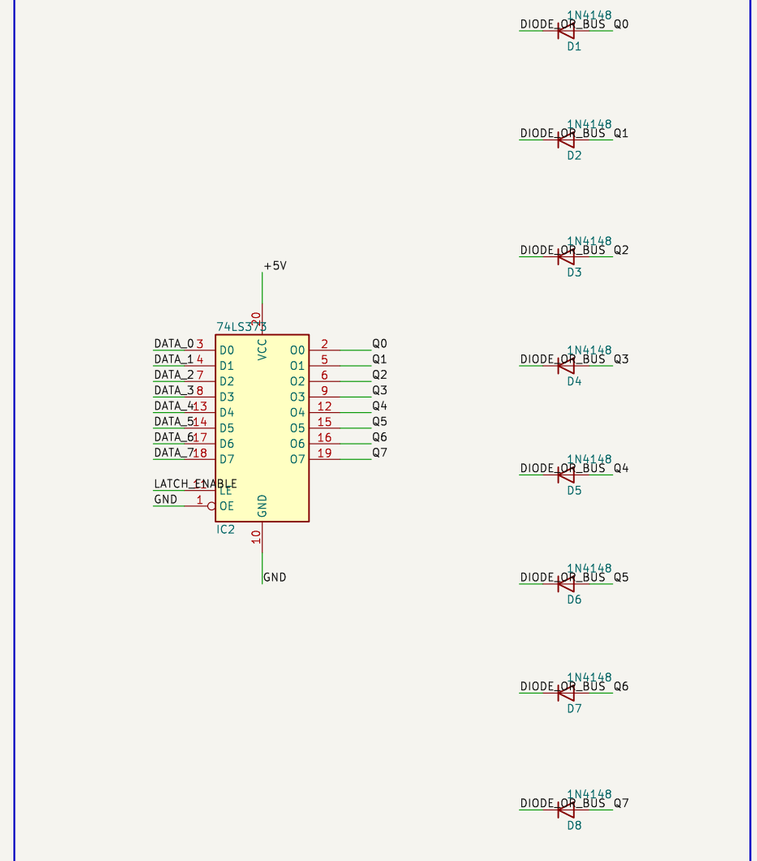

MountingHole_M3
H1

MountingHole_M3
H2

MountingHole_M3
H3

MountingHole_M3
H4

8-Player Quiz Buzzer with 74LS373 & Regulated 5V Power Supply
Faculty: Dr. Eswaramoorthy K V
Mid Semester Practical Examination
Author: Divyansh Rawat (Roll No: 124EC0030)
IIITDM Kurnool – Dept of ECE | EPM Laboratory

Sheet: /
File: school_college_quiz_buzzer.kicad_sch

Title: School/College Quiz Buzzer (8 Players)

Size: A3	Date: 2026-11-11	**Rev: v1.0**
KiCad E.D.A. 9.0.8		Id: 1/1